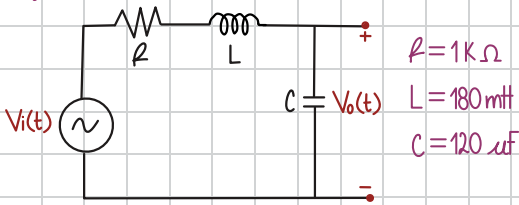


Ejercicios.



① Hallar E.D.O

Si $V_o(t) = V_c(t) = \frac{1}{C} \int_0^t i(\tau) d\tau$

$i_c(t) = C \frac{d}{dt} V_c(t)$

$V_L(t) = L \frac{d}{dt} i_L(t)$

$V_R(t) = R i_R(t)$

Como están en serie: $i(t) = i_R(t) = i_L(t) = i_C(t)$

$V_i(t) = V_R(t) + V_L(t) + V_C(t)$

$V_i(t) = R \cdot C \frac{d}{dt} V_c(t) + L \frac{d}{dt} \left(C \frac{d}{dt} V_c(t) \right) + V_c(t)$

$V_i(t) = RC \frac{d}{dt} V_c(t) + LC \frac{d^2}{dt^2} V_c(t) + V_c(t)$

$V_i(t) = LC \frac{d^2}{dt^2} V_c(t) + RC \frac{d}{dt} V_c(t) + V_c(t) \rightarrow \text{E.D.O del circuito RLC}$

② Hallar la función de transferencia y diagrama de bode [dB]

$H(w) = \frac{Y(w)}{X(w)} = \frac{V_o(w)}{V_i(w)}$

$V_o(t) = V_c(t) = \frac{1}{C} \int_0^t i(\tau) d\tau$

$V_i(t) = LC \frac{d^2}{dt^2} V_c(t) + RC \frac{d}{dt} V_c(t) + V_c(t)$

$FF\{LC \frac{d^2}{dt^2} V_c(t)\} = LC FF\{\frac{d^2}{dt^2} V_c(t)\} = LC(jw)^2 V_c(w)$

$FF\{RC \frac{d}{dt} V_c(t)\} = RC FF\{\frac{d}{dt} V_c(t)\} = RC jw V_c(w)$

$FF\{V_c(t)\} = V_c(w)$

$H(w) = \frac{1}{(1 - LCw^2) + jRCw}$

$H(w) = \frac{1}{(1 - LCw^2) + jRCw}$ función de transferencia

Para el diagrama de bode [dB]

$V_i(w) = LC(jw)^2 V_c(w) + RC(jw) V_c(w) + V_c(w)$

Si $V_o(t) = V_c(t)$

$V_i(w) = (LC(jw)^2 + RC(jw) + 1) V_c(w)$

$\frac{1}{(LC(jw)^2 + RC(jw) + 1)} = \frac{V_o(w)}{V_i(w)} = H(w)$

$\frac{1}{(-LCw^2 + RC(jw) + 1)} = H(w)$

$\frac{1}{(1 - LCw^2) + jRCw} = H(w)$

$|H(w)| = \frac{1}{\sqrt{(1 - LCw^2)^2 + (RCw)^2}}$

Magnitud en dB

$|H(w)|_{dB} = 20 \log_{10} \left(\frac{1}{\sqrt{(1 - LCw^2)^2 + (RCw)^2}} \right)$

③ Hallar $H(s) = \frac{Y(s)}{X(s)} = \frac{V_0(s)}{V_i(s)}$ y diagrama de polos y ceros

$$V_i(t) = LC \frac{d^2 V_c(t)}{dt^2} + RC \frac{dV_c(t)}{dt} + V_c(t)$$

→ Ahora en el dominio de s

$$\mathcal{L}\{V_i(t)\} = V_i(s)$$

$$\mathcal{L}\{LC \frac{d^2 V_c(t)}{dt^2}\} = LC s^2 V_c(s)$$

$$\mathcal{L}\{RC \frac{dV_c(t)}{dt}\} = RC s V_c(s)$$

$$\mathcal{L}\{V_c(t)\} = V_c(s)$$

$$V_i(s) = LC s^2 V_c(s) + RC s V_c(s) + V_c(s)$$

$$\text{Si } V_0(s) = V_c(s)$$

$$V_i(s) = (LC s^2 + RC s + 1) V_0(s)$$

$$\frac{1}{(LC s^2 + RC s + 1)} = \frac{V_0(s)}{V_i(s)}$$

$$H(s) = \frac{1}{(LC s^2 + RC s + 1)} \quad \text{función de transferencia}$$

Ceros → Raíces del numerador (Son las s donde $H(s) = 0$)

Polos → Raíces del denominador (Son las s donde $H(s) \rightarrow \infty$)

• No hay ceros

• Polos: $LC s^2 + RC s + 1 = 0$

$$2,16 \times 10^{-5} s^2 + 0,12 s + 1 = 0$$

Polos en $-8,3459$ y $-5547,2097$

$$s_{1,2} = \frac{-0,12 \pm \sqrt{(0,12)^2 - 4 \cdot 2,16 \times 10^{-5}}}{2 \cdot 2,16 \times 10^{-5}}$$

$$s_1 = -8,3459$$

$$s_2 = -5547,2097$$

④ Hallar $h(t)$ desde ③ $X(t) = \delta(t)$ $X(s) = \mathcal{L}\{\delta(t)\}$
 $H(s) = Y(s)$ $h(t) = \mathcal{L}^{-1}\{H(s)\}$

$$\text{Si } X(s) = \mathcal{L}\{\delta(t)\} = 1$$

$$H(s) = \frac{Y(s)}{X(s)} = \frac{Y(s)}{1} = Y(s)$$

$$s_1 = -8,3459$$

$$s_2 = -5547,2097$$

$$H(s) = \frac{1}{2,16 \times 10^{-5} s^2 + 0,12 s + 1} = \frac{1}{2,16 \times 10^{-5} (s + 8,3459)(s + 5547,2097)} = \frac{1}{2,16 \times 10^{-5}} \left(\frac{A}{s + 8,3459} + \frac{B}{s + 5547,2097} \right)$$

$$1 = A(s + 5547,2097) + B(s + 8,3459)$$

$$\text{Si } s = s_1 \quad A = \frac{1}{-8,3459 + 5547,2097} = \frac{1}{5538,8638} = 1,80542 \times 10^{-4}$$

$$s = s_2 \quad B = \frac{1}{-5547,2097 + 8,3459} = -A = -1,80542 \times 10^{-4}$$

$$H(s) = \frac{1}{2,16 \times 10^{-5}} \left(\frac{A}{s + 8,3459} + \frac{-A}{s + 5547,2097} \right) = A \frac{1}{2,16 \times 10^{-5}} \left(\frac{1}{s + 8,3459} - \frac{1}{s + 5547,2097} \right)$$

$$\mathcal{L}^{-1}\left\{\frac{1}{s-a}\right\} = e^{at} u(t)$$

$$h(t) = \mathcal{L}^{-1}\{H(s)\} = A \frac{1}{2,16 \times 10^{-5}} (\mathcal{L}^{-1}\left\{\frac{1}{s + 8,3459}\right\} - \mathcal{L}^{-1}\left\{\frac{1}{s + 5547,2097}\right\}) = \frac{1,80542 \times 10^{-4}}{2,16 \times 10^{-5}} (e^{-8,3459t} u(t) - e^{-5547,2097t} u(t))$$

$$= 8,3584 u(t) (e^{-8,3459t} - e^{-5547,2097t})$$

⑤ Hallar $h(t)$ desde ③ $X(s) = \delta(s)$ $X(s) = \mathcal{L}\{\delta(t)\}$
 $H(s) = Y(s)$ $h(t) = \mathcal{L}^{-1}\{H(s)\}$

$$Y(s) = H(s)X(s) = H(s)\mathcal{L}\{u(t)\}$$

$$Y(s) = \mathcal{L}^{-1}\{H(s)\mathcal{L}\{u(t)\}\} : \delta \quad X(s) = \mathcal{L}\{u(t)\} = \frac{1}{s} \quad y \quad H(s) = \frac{1}{2,16 \times 10^{-5} (s+8,3459)(s+5547,2097)}$$

$$Y(s) = \frac{1}{s} \cdot \frac{1}{2,16 \times 10^{-5} (s+8,3459)(s+5547,2097)} = \frac{1}{2,16 \times 10^{-5}} \left(\frac{A}{s} + \frac{B}{s+8,3459} + \frac{C}{s+5547,2097} \right)$$

$$A = \frac{1}{1} = 1 \quad B = \frac{8,3584}{-8,3459} \approx -1 \quad C = \frac{-8,3584}{-5547,2097} \approx 0,001057$$

$$Y(s) = \mathcal{L}^{-1} \left\{ \frac{1}{2,16 \times 10^{-5}} \left(\frac{1}{s} - \frac{1}{s+8,3459} + \frac{0,001057}{s+5547,2097} \right) \right\}$$

$$Y(t) = \frac{1}{2,16 \times 10^{-5}} \cdot u(t) (e^0 - e^{-8,3459t} + 0,001057 e^{-5547,2097t})$$